

RCSJ model using python

Felix Schmidt¹

Kavli Institute of NanoScience, Delft University of Technology, Lorentzweg 1, 2628 CJ, Delft, The Netherlands.

(Dated: December 8, 2017)

I. CURRENT BIASING

We model the Josephson junction in the simplest way possible: A series network of a resistor R , a capacitor C and a nonlinear inductor. The total current running through the network is

$$I(t) = I_s(t) + I_R(t) + I_C(t) \quad (1)$$

$$I(t) = I_c \sin(\phi) + \frac{V}{R} + C \frac{dV}{dt} \quad (2)$$

$$V(t) = \frac{\hbar}{2e} \frac{d\phi}{dt} \quad (3)$$

$$\frac{dV}{dt} = \frac{\hbar}{2e} \frac{d^2\phi}{dt^2} \quad (4)$$

The equation is simplified with normalized time $\tau = \omega_p t$, where $\omega_p = \sqrt{\frac{2eI_c}{\hbar C}}$ and quality factor $Q = \omega_p RC$ to

$$\frac{d^2\gamma}{d\tau^2} + \frac{1}{Q} \frac{d\gamma}{d\tau} + \sin(\gamma) = \frac{I}{I_c} \quad (5)$$

We can define two regimes: The **overdamped** case for $Q \ll 1$, and the **underdamped** case for $Q \gg 1$:

$$Q \ll 1 : \frac{d\gamma}{d\tau} \approx \frac{I}{I_c} - \sin(\gamma) \rightarrow V = R\sqrt{I^2 - I_c^2} \quad (6)$$

$$Q \gg 1 : \frac{d^2\gamma}{d\tau^2} \approx \frac{2e}{\hbar} V + const. \rightarrow V = RI \quad (7)$$

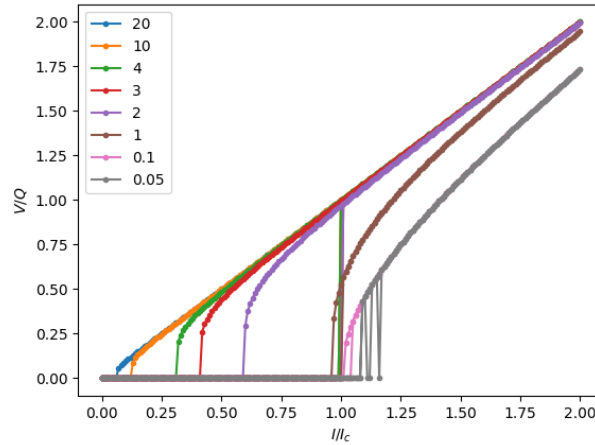


Figure 1. Current-voltage curves for various damping cases. As predicted by theory, high damping ($Q \ll 1$) corresponds to a square-root like IVC with no hysteresis, while low damping ($Q \gg 1$) results in strong hysteresis with a almost linear retrapping branch.

II. VOLTAGE BIASING

REFERENCES